 


NANO PROCESSOR

Developed By :

- Gathsara J.A.S. - 210180L
- Gallage D. - 210173T

Group Number - 30



LAB TASK

- design and develop a 4-bit arithmetic unit that can add and subtract signed integers.
- decode instructions to activate necessary components on the processor.
- design and develop k-way b-bit multiplexers or tri-state busses.
- verify their functionality via simulation and on the development board.


ASSEMBLY PROGRAM

```
MOVI R7, 0
MOVI R1, 1
MOVI R2, 2
MOVI R3, 3
ADD  R7, R1
ADD  R7, R2
ADD  R7, R3
JZR  R0, 7
```

MACHINE CODE REPRESENTATION

```
101110000000
100010000001
100100000010
100110000011
001110010000
001110100000
001110110000
110000000111
```

VHDL FILES AND TIMING DIAGRAMS

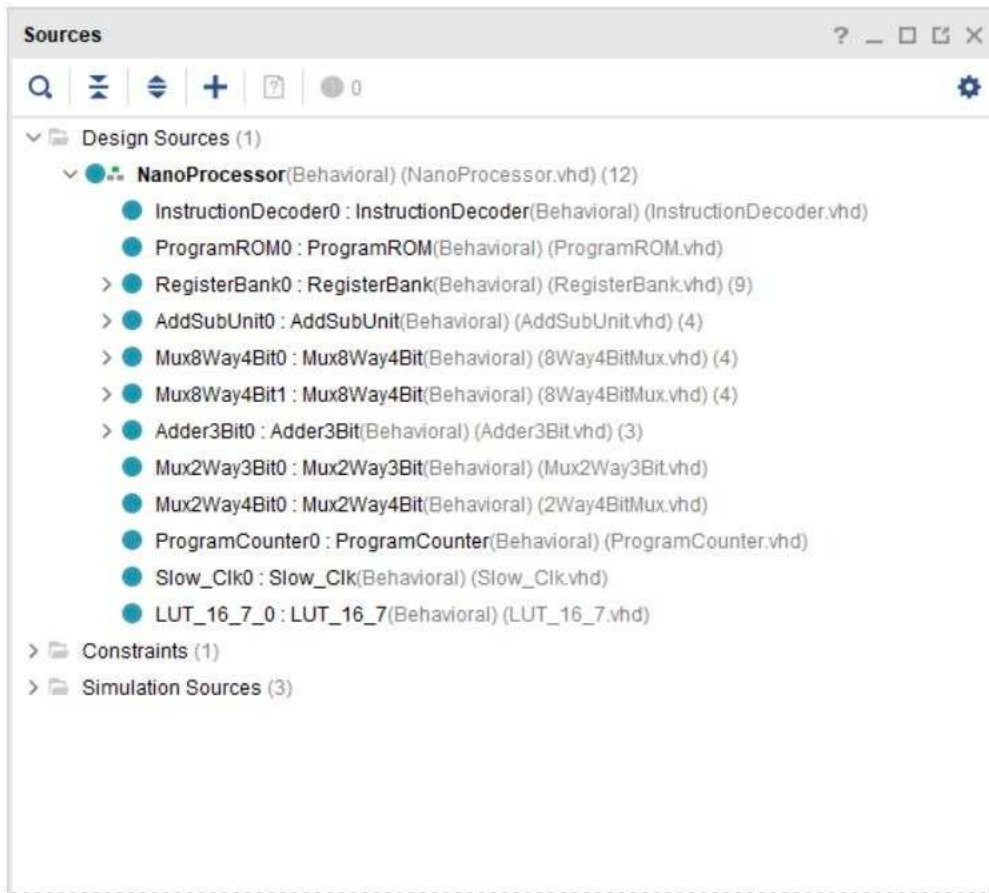

Design Sources

Nano Processor

NANOPROCESSOR.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity NanoProcessor is
  Port ( Clk : in STD_LOGIC;
        Reset : in STD_LOGIC; -- Reset button
        Reg7 : out STD_LOGIC_VECTOR (3 downto 0); -- To Reg7 LED
        Zero : out STD_LOGIC; -- To zero LED
        Overflow : out STD_LOGIC; -- To overflow led
        SevenSegment : out STD_LOGIC_VECTOR(6 downto 0); -- To seven Segment
        AnodeSelect : out STD_LOGIC_VECTOR (3 downto 0); -- To Anode Select Bus
        SwitchIn : in STD_LOGIC_VECTOR(3 downto 0);
        RegDisplay : in STD_LOGIC_VECTOR(2 downto 0));
end NanoProcessor;
```

architecture Behavioral of NanoProcessor is

```
Component InstructionDecoder port(  
    InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);  
    RegisterCheck : in STD_LOGIC_VECTOR (3 downto 0);  
    JumpAddress : out STD_LOGIC_VECTOR (2 downto 0);  
    AddSubSelect : out STD_LOGIC;  
    RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);  
    LoadSelect : out STD_LOGIC;  
    ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);  
    RegASelect : out STD_LOGIC_VECTOR (2 downto 0);  
    RegBSelect : out STD_LOGIC_VECTOR (2 downto 0);  
    JumpFlag : out STD_LOGIC;  
    SwitchIn : in STD_LOGIC_VECTOR(3 downto 0));  
end component;  
  
component ProgramROM port(  
    MemorySelect : in STD_LOGIC_VECTOR (2 downto 0);  
    InstructionBus : out STD_LOGIC_VECTOR (11 downto 0));  
end component;  
  
component RegisterBank port(  
    RegisterIn : in STD_LOGIC_VECTOR (3 downto 0);  
    Clk : in STD_LOGIC;  
    output0 : out STD_LOGIC_VECTOR (3 downto 0);  
    output1 : out STD_LOGIC_VECTOR (3 downto 0);  
    output2 : out STD_LOGIC_VECTOR (3 downto 0);  
    output3 : out STD_LOGIC_VECTOR (3 downto 0);  
    output4 : out STD_LOGIC_VECTOR (3 downto 0);  
    output5 : out STD_LOGIC_VECTOR (3 downto 0);  
    output6 : out STD_LOGIC_VECTOR (3 downto 0);  
    output7 : out STD_LOGIC_VECTOR (3 downto 0);  
    RegisterEn : in STD_LOGIC_VECTOR (2 downto 0);  
    Reset : in STD_LOGIC := '0');  
end component;  
  
component AddSubUnit port(  
    A : in STD_LOGIC_VECTOR (3 downto 0);  
    B : in STD_LOGIC_VECTOR (3 downto 0);  
    S : out STD_LOGIC_VECTOR (3 downto 0);  
    AddSubSelect : in STD_LOGIC;  
    Overflow : out STD_LOGIC;  
    Zero : out STD_LOGIC);  
end component;  
  
component Mux8Way4Bit port(  
    In0 : in STD_LOGIC_VECTOR (3 downto 0);  
    In1 : in STD_LOGIC_VECTOR (3 downto 0);  
    In2 : in STD_LOGIC_VECTOR (3 downto 0);  
    In3 : in STD_LOGIC_VECTOR (3 downto 0);
```

```

    In4 : in STD_LOGIC_VECTOR (3 downto 0);
    In5 : in STD_LOGIC_VECTOR (3 downto 0);
    In6 : in STD_LOGIC_VECTOR (3 downto 0);
    In7 : in STD_LOGIC_VECTOR (3 downto 0);
    OutMux : out STD_LOGIC_VECTOR (3 downto 0);
    Control : in STD_LOGIC_VECTOR (2 downto 0));
end component;

component Adder3Bit port(
    A : in STD_LOGIC_VECTOR (2 downto 0);
    B : in STD_LOGIC_VECTOR (2 downto 0);
    output : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Mux2Way3Bit port(
    In0 : in STD_LOGIC_VECTOR (2 downto 0);
    In1 : in STD_LOGIC_VECTOR (2 downto 0);
    LoadSelect : in STD_LOGIC;
    output : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Mux2Way4Bit port(
    In0 : in STD_LOGIC_VECTOR (3 downto 0);
    In1 : in STD_LOGIC_VECTOR (3 downto 0);
    LoadSelect : in STD_LOGIC;
    output : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component ProgramCounter port(
    input : in STD_LOGIC_VECTOR (2 downto 0);
    output : out STD_LOGIC_VECTOR (2 downto 0);
    Clk : in STD_LOGIC;
    Reset : in STD_LOGIC);
end component;

component Slow_Clk port(
    Clk_in : in STD_LOGIC;
    Clk_out : out STD_LOGIC);
end component;

Component LUT_16_7 port (
    address : in STD_LOGIC_VECTOR (3 downto 0);
    data : out STD_LOGIC_VECTOR (6 downto 0));
End component;

SIGNAL InstructionBus : std_logic_vector(11 downto 0);
SIGNAL Mux8Way4BitOut0, Mux8Way4BitOut1, ImmediateValue, RegisterIn, AddSubOut,
lookupTableIn : std_logic_vector(3 downto 0);
SIGNAL JumpAddress, RegisterEnable, RegASelect, RegBSelect, ROMMemorySelect, Adder3BitOut,
ProgramCounterIn : std_logic_vector(2 downto 0);
SIGNAL AddSubSelect, LoadSelect, JumpFlag, SlowClock: std_logic;

```

```

SIGNAL DataBus0, DataBus1, DataBus2, DataBus3, DataBus4, DataBus5, DataBus6, DataBus7 :
std_logic_vector(3 downto 0);

Signal S_temp : std_logic_vector(3 downto 0);

signal count2 : integer := 1;
--signal count3 : std_logic := '0';

begin

InstructionDecoder0 : InstructionDecoder port map(
    InstructionBus => InstructionBus,
    RegisterCheck => Mux8Way4BitOut0,
    JumpAddress => JumpAddress,
    AddSubSelect => AddSubSelect,
    RegisterEnable => RegisterEnable,
    LoadSelect => LoadSelect,
    ImmediateValue => ImmediateValue,
    RegASelect => RegASelect,
    RegBSelect => RegBSelect,
    JumpFlag => JumpFlag,
    SwitchIn => SwitchIn
);

ProgramROM0 : ProgramROM port map(
    MemorySelect => ROMMemorySelect,
    InstructionBus => InstructionBus
);

RegisterBank0 : RegisterBank port map(
    RegisterIn => RegisterIn,
    Clk => SlowClock,
    output0 => DataBus0,
    output1 => DataBus1,
    output2 => DataBus2,
    output3 => DataBus3,
    output4 => DataBus4,
    output5 => DataBus5,
    output6 => DataBus6,
    output7 => DataBus7,
    RegisterEn => RegisterEnable,
    Reset => Reset
);

AddSubUnit0 : AddSubUnit port map(
    A => Mux8Way4BitOut0,
    B => Mux8Way4BitOut1,
    S => AddSubOut,
    AddSubSelect => AddSubSelect,

```

```

        Overflow => Overflow,
        Zero => Zero
    );

Mux8Way4Bit0 : Mux8Way4Bit port map(
    In0 => DataBus0,
    In1 => DataBus1,
    In2 => DataBus2,
    In3 => DataBus3,
    In4 => DataBus4,
    In5 => DataBus5,
    In6 => DataBus6,
    In7 => DataBus7,
    OutMux => Mux8Way4BitOut0,
    Control => RegASelect
);

Mux8Way4Bit1 : Mux8Way4Bit port map(
    In0 => DataBus0,
    In1 => DataBus1,
    In2 => DataBus2,
    In3 => DataBus3,
    In4 => DataBus4,
    In5 => DataBus5,
    In6 => DataBus6,
    In7 => DataBus7,
    OutMux => Mux8Way4BitOut1,
    Control => RegBSelect
);

Adder3Bit0 : Adder3Bit port map(
    A => ROMMemorySelect,
    B => "001",
    output => Adder3BitOut
);

Mux2Way3Bit0 : Mux2Way3Bit port map(
    In0 => Adder3BitOut,
    In1 => JumpAddress,
    LoadSelect => JumpFlag,
    output => ProgramCounterIn
);

Mux2Way4Bit0 : Mux2Way4Bit port map(
    In0 => ImmediateValue,
    In1 => AddSubOut,
    LoadSelect => LoadSelect,
    output => RegisterIn
);

ProgramCounter0 : ProgramCounter port map(

```

```

        input => ProgramCounterIn,
        output => ROMMemorySelect,
        Clk => SlowClock,
        Reset => Reset
    );

    Slow_Clk0 : Slow_Clk port map(
        Clk_in => Clk,
        Clk_out => SlowClock
    );

    LUT_16_7_0 : LUT_16_7 port map(
        address => S_temp,
        data => SevenSegment
    );

    Reg7 <= DataBus7;

    process(Clk)
    begin

        if(rising_edge(Clk)) then
            count2 <= count2 + 1;
            if (count2 = 10000) then -- Register Value Display
                AnodeSelect <= "1110";
                case RegDisplay is
                    when "000" =>
                        S_temp <= DataBus0;
                    when "001" =>
                        S_temp <= DataBus1;
                    when "010" =>
                        S_temp <= DataBus2;
                    when "011" =>
                        S_temp <= DataBus3;
                    when "100" =>
                        S_temp <= DataBus4;
                    when "101" =>
                        S_temp <= DataBus5;
                    when "110" =>
                        S_temp <= DataBus6;
                    when "111" =>
                        S_temp <= DataBus7;
                end case;

            elsif (count2 = 20000) then -- RegisterDisplay number display
                AnodeSelect <= "0111";
                lookupTableIn(3) <= '0';
                lookupTableIn(2 downto 0) <= RegDisplay;
                S_temp <= lookupTableIn;
            elsif (count2 = 30000) then -- Counter
                AnodeSelect <= "1101";

```



```

        lookupTableIn(3) <= '0';
        lookupTableIn(2 downto 0) <= ROMMemorySelect;
        S_temp <= lookupTableIn;
        count2 <= 0;
    end if;
end if;
end process;

end Behavioral;

```

Instruction Decoder

INSTRUCTIONDECODER.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity InstructionDecoder is
    Port ( InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);
          RegisterCheck : in STD_LOGIC_VECTOR (3 downto 0);
          JumpAddress : out STD_LOGIC_VECTOR (2 downto 0);
          AddSubSelect : out STD_LOGIC;
          RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
          LoadSelect : out STD_LOGIC;
          ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);
          RegASelect : out STD_LOGIC_VECTOR (2 downto 0);
          RegBSelect : out STD_LOGIC_VECTOR (2 downto 0);
          JumpFlag : out STD_LOGIC;
          SwitchIn : in STD_LOGIC_VECTOR (3 downto 0));
end InstructionDecoder;

architecture Behavioral of InstructionDecoder is

begin
    process (InstructionBus(11 downto 0),RegisterCheck,SwitchIn)
    begin
        if (InstructionBus(11 downto 10) = "00") then -- Add
            RegASelect <= InstructionBus(9 downto 7);
            RegBSelect <= InstructionBus(6 downto 4);
            AddSubSelect <= '0';
            LoadSelect <= '1';
            RegisterEnable <= InstructionBus(9 downto 7);
            JumpFlag <= '0';

            elsif (InstructionBus(11 downto 10) = "01") then -- Negative
                RegBSelect <= InstructionBus(9 downto 7);
                RegisterEnable <= InstructionBus(9 downto 7);
                LoadSelect <= '1';

```

```

        RegASelect <= "000";
        AddSubSelect <= '1';
        JumpFlag <= '0';

    elsif (InstructionBus(11 downto 10) = "10") then -- Move
        RegisterEnable <= InstructionBus(9 downto 7);
        LoadSelect <= '0';
        JumpFlag <= '0';
        if (InstructionBus(5) = '0') then
            ImmediateValue <= InstructionBus(3 downto 0);
        else
            ImmediateValue <= SwitchIn;
        end if;

    else
        JumpAddress <= InstructionBus(2 downto 0); -- Jump
        RegASelect <= InstructionBus(9 downto 7);
        RegisterEnable <= "000";

        if RegisterCheck = "0000" then
            JumpFlag <= '1';
        else
            JumpFlag <= '0';
        end if;

    end if;
end process;

end Behavioral;

```

Program ROM

PROGRAMROM.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity ProgramROM is
    Port ( MemorySelect : in STD_LOGIC_VECTOR (2 downto 0);
          InstructionBus : out STD_LOGIC_VECTOR (11 downto 0));
end ProgramROM;

architecture Behavioral of ProgramROM is

```

```

type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);

signal program_ROM : rom_type := (
    "101110000000", -- 0 MOVI R7,0
    "100010000001", -- 1 MOVI R1,1
    "100100000010", -- 2 MOVI R2,2
    "100110000011", -- 3 MOVI R3,3
    "001110010000", -- 4 ADD R7,R1
    "001110100000", -- 5 ADD R7,R2
    "001110110000", -- 6 ADD R7,R3
    "110000000111"); -- 7 JZR R0,7

begin

    InstructionBus <= program_ROM(to_integer(unsigned(MemorySelect)));

end Behavioral;

```

Register Bank

REGISTERBANK.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RegisterBank is
    Port ( RegisterIn : in STD_LOGIC_VECTOR (3 downto 0);
          Clk : in STD_LOGIC;
          output0 : out STD_LOGIC_VECTOR (3 downto 0);
          output1 : out STD_LOGIC_VECTOR (3 downto 0);
          output2 : out STD_LOGIC_VECTOR (3 downto 0);
          output3 : out STD_LOGIC_VECTOR (3 downto 0);
          output4 : out STD_LOGIC_VECTOR (3 downto 0);
          output5 : out STD_LOGIC_VECTOR (3 downto 0);
          output6 : out STD_LOGIC_VECTOR (3 downto 0);
          output7 : out STD_LOGIC_VECTOR (3 downto 0);
          RegisterEn : in STD_LOGIC_VECTOR (2 downto 0);
          Reset : in STD_LOGIC := '0');
end RegisterBank;

architecture Behavioral of RegisterBank is

    component Reg port(
        D : in STD_LOGIC_VECTOR (3 downto 0);
        En : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0);
        Reset : in STD_LOGIC);
    end component;

```

```

component Decoder_3_to_8 port(
    I : in STD_LOGIC_VECTOR (2 downto 0);
    EN : in STD_LOGIC;
    Y : out STD_LOGIC_VECTOR (7 downto 0));

end component;

SIGNAL Y0 : std_logic_vector(7 downto 0);
SIGNAL HC : std_logic_vector(3 downto 0);
Signal reset0 : std_logic;

begin

Decoder : Decoder_3_to_8 port map(
    I => RegisterEn,
    EN => '1',
    Y => Y0 );

Reg0 : Reg port map(
    D => HC,          -- Hardcoded
    En => '1',
    Clk => Clk,
    Q => output0,
    Reset => reset0 );

Reg1 : Reg port map(
    D => RegisterIn,
    En => Y0(1),
    Clk => Clk,
    Q => output1,
    Reset => reset0 );

Reg2 : Reg port map(
    D => RegisterIn,
    En => Y0(2),
    Clk => Clk,
    Q => output2,
    Reset => reset0 );

Reg3 : Reg port map(
    D => RegisterIn,
    En => Y0(3),
    Clk => Clk,
    Q => output3,
    Reset => reset0 );

Reg4 : Reg port map(
    D => RegisterIn,
    En => Y0(4),

```

```
    Clk => Clk,  
    Q => output4,  
    Reset => reset0 );  
  
Reg5 : Reg port map(  
    D => RegisterIn,  
    En => Y0(5),  
    Clk => Clk,  
    Q => output5,  
    Reset => reset0 );  
  
Reg6 : Reg port map(  
    D => RegisterIn,  
    En => Y0(6),  
    Clk => Clk,  
    Q => output6,  
    Reset => reset0 );  
  
Reg7 : Reg port map(  
    D => RegisterIn,  
    En => Y0(7),  
    Clk => Clk,  
    Q => output7,  
    Reset => reset0 );  
  
HC <= "0000";  
reset0 <= Reset;  
  
end Behavioral;
```

DECODER_3_TO_8.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is

    component decoder_2_to_4 port(
        I : in STD_LOGIC_VECTOR;
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR );
    end component;

    signal I0, I1 : STD_LOGIC_VECTOR(1 downto 0);
    signal Y0, Y1 : STD_LOGIC_VECTOR(3 downto 0);
    signal en0, en1 : STD_LOGIC;

begin

    Decoder_2_to_4_0 : Decoder_2_to_4 port map(
        I => I0,
        EN => en0,
        Y => Y0 );

    Decoder_2_to_4_1 : Decoder_2_to_4 port map(
        I => I1,
        EN => en1,
        Y => Y1 );

    en0 <= NOT(I(2)) AND EN;
    en1 <= I(2) AND EN;
    I0 <= I(1 downto 0);
    I1 <= I(1 downto 0);
    Y(3 downto 0) <= Y0;
    Y(7 downto 4) <= Y1;

end Behavioral
```

DECODER_2_TO_4.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_2_to_4 is
    Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (3 downto 0));
end Decoder_2_to_4;

architecture Behavioral of Decoder_2_to_4 is

begin
    Y(0) <= NOT(I(0)) AND NOT(I(1)) AND EN;
    Y(1) <= I(0) AND NOT(I(1)) AND EN;
    Y(2) <= NOT(I(0)) AND I(1) AND EN;
    Y(3) <= I(0) AND I(1) AND EN;

end Behavioral;
```

REG.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC := '1';
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0) := "0000";
          Reset : in STD_LOGIC := '0');
end Reg;

architecture Behavioral of Reg is

begin
    process (Clk) begin
        if (rising_edge(Clk)) then
            if Reset = '1' then
                Q <= "0000";
            elsif En = '1' then
                Q <= D;
            end if;
        end if;
    end process;

end Behavioral;
```

Add Sub Unit

ADDSUBUNIT.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity AddSubUnit is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          S : out STD_LOGIC_VECTOR (3 downto 0);
          AddSubSelect : in STD_LOGIC;
          Overflow : out STD_LOGIC;
          Zero : out STD_LOGIC);
end AddSubUnit;

architecture Behavioral of AddSubUnit is

    component FA
        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              C_in : in STD_LOGIC;
              S : out STD_LOGIC;
              C_out : out STD_LOGIC);
    end component;

    SIGNAL B2,S2 : std_logic_vector(3 downto 0);
    SIGNAL C2 : std_logic_vector(2 downto 0);

begin

    FA_0 : FA port map(
        A => A(0),
        B => B2(0),
        C_in => AddSubSelect,
        S => S2(0),
        C_out => C2(0)
    );

    FA_1 : FA port map(
        A => A(1),
        B => B2(1),
        C_in => C2(0),
        S => S2(1),
        C_out => C2(1)
    );

    FA_2 : FA port map(
        A => A(2),
```



```

    B => B2(2),
    C_in => C2(1),
    S => S2(2),
    C_out => C2(2)
);

FA_3 : FA port map(
    A => A(3),
    B => B2(3),
    C_in => C2(2),
    S => S2(3),
    C_out => Overflow
);

B2(0) <= AddSubSelect XOR B(0);
B2(1) <= AddSubSelect XOR B(1);
B2(2) <= AddSubSelect XOR B(2);
B2(3) <= AddSubSelect XOR B(3);

S <= S2;

Zero <= NOT(S2(0) OR S2(1) OR S2(2) OR S2(3));

end Behavioral;

```

FA.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FA is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C_in : in STD_LOGIC;
          S : out STD_LOGIC;
          C_out : out STD_LOGIC);
end FA;

architecture Behavioral of FA is

    component HA port (
        A : in std_logic;
        B : in std_logic;
        S : out std_logic;
        C : out std_logic);
    end component;

    SIGNAL HA0_S, HA0_C, HA1_S, HA1_C : std_logic;

begin

```

```

HA_0 : HA port map (
  A => A,
  B => B,
  S => HA0_S,
  C => HA0_C );

HA_1 : HA port map (
  A => HA0_S,
  B => C_in,
  S => HA1_S,
  C => HA1_C );

S <= HA1_S;
C_out <= HA0_C OR HA1_C;

end Behavioral;

```

HA.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity HA is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        S : out STD_LOGIC;
        C : out STD_LOGIC);
end HA;

architecture Behavioral of HA is

begin
  S <= A XOR B;
  C <= A AND B;

end Behavioral;

```

Mux 8 Way 4 Bit

MUX8WAY4BIT.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux8Way4Bit is
  Port ( In0 : in STD_LOGIC_VECTOR (3 downto 0);
        In1 : in STD_LOGIC_VECTOR (3 downto 0);
        In2 : in STD_LOGIC_VECTOR (3 downto 0);

```

```

    In3 : in STD_LOGIC_VECTOR (3 downto 0);
    In4 : in STD_LOGIC_VECTOR (3 downto 0);
    In5 : in STD_LOGIC_VECTOR (3 downto 0);
    In6 : in STD_LOGIC_VECTOR (3 downto 0);
    In7 : in STD_LOGIC_VECTOR (3 downto 0);
    OutMux : out STD_LOGIC_VECTOR (3 downto 0);
    Control : in STD_LOGIC_VECTOR (2 downto 0));
end Mux8Way4Bit;

```

architecture Behavioral of Mux8Way4Bit is

```

component Mux_8_to_1
  Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
        D : in STD_LOGIC_VECTOR (7 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC);
end component;

```

```

SIGNAL Control0 : std_logic_vector(2 downto 0);

```

```

begin

```

```

Mux_8_to_1_A : Mux_8_to_1
  port map(
    S => Control0,

    D(0) => In0(0),
    D(1) => In1(0),
    D(2) => In2(0),
    D(3) => In3(0),
    D(4) => In4(0),
    D(5) => In5(0),
    D(6) => In6(0),
    D(7) => In7(0),

    EN => '1',
    Y => OutMux(0)
  );

```

```

Mux_8_to_1_B : Mux_8_to_1
  port map(
    S => Control0,

    D(0) => In0(1),
    D(1) => In1(1),
    D(2) => In2(1),
    D(3) => In3(1),
    D(4) => In4(1),
    D(5) => In5(1),
    D(6) => In6(1),
    D(7) => In7(1),

```

```

        EN => '1',
        Y => OutMux(1)
    );

Mux_8_to_1_C : Mux_8_to_1
    port map(
        S => Control0,

        D(0) => In0(2),
        D(1) => In1(2),
        D(2) => In2(2),
        D(3) => In3(2),
        D(4) => In4(2),
        D(5) => In5(2),
        D(6) => In6(2),
        D(7) => In7(2),

        EN => '1',
        Y => OutMux(2)
    );

Mux_8_to_1_D : Mux_8_to_1
    port map(
        S => Control0,

        D(0) => In0(3),
        D(1) => In1(3),
        D(2) => In2(3),
        D(3) => In3(3),
        D(4) => In4(3),
        D(5) => In5(3),
        D(6) => In6(3),
        D(7) => In7(3),

        EN => '1',
        Y => OutMux(3)
    );

Control0 <= Control;

end Behavioral;

```

MUX_8_TO_1.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_8_to_1 is
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);

```

```

        D : in STD_LOGIC_VECTOR (7 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC);
end Mux_8_to_1;

architecture Behavioral of Mux_8_to_1 is

component Decoder_3_to_8 port(
    I    : in STD_LOGIC_VECTOR;
    EN   : in STD_LOGIC;
    Y    : out STD_LOGIC_VECTOR);
end component;

signal Dec_out, And_out : STD_LOGIC_VECTOR(7 downto 0);
signal Or_out : STD_LOGIC;

begin

Decoder_3_to_8_0 : Decoder_3_to_8 port map(
    I => S,
    EN => EN,
    Y => Dec_out );

    And_out <= Dec_out AND D;
    Or_out <= And_out(0) OR And_out(1) OR And_out(2) OR And_out(3) OR
        And_out(4) OR And_out(5) OR And_out(6) OR And_out(7);
    Y <= EN and Or_out;

end Behavioral;

```

(Decoder3to8 added previously)

Adder 3 bit

ADDER3BIT.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Adder3Bit is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          B : in STD_LOGIC_VECTOR (2 downto 0);
          output : out STD_LOGIC_VECTOR (2 downto 0));
end Adder3Bit;

architecture Behavioral of Adder3Bit is

component FA port (
    A : in std_logic;

```

```

    B : in std_logic;
    C_in : in STD_LOGIC;
    S : out STD_LOGIC;
    C_out : out STD_LOGIC);
end component;

SIGNAL FA_C : std_logic_vector(2 downto 0);

begin

FA_0 : FA port map (
    A => A(0),
    B => B(0),
    S => output(0),
    C_in => '0',
    C_out => FA_C(0));

FA_1 : FA port map (
    A => A(1),
    B => B(1),
    S => output(1),
    C_in => FA_C(0),
    C_out => FA_C(1));

FA_2 : FA port map (
    A => A(2),
    B => B(2),
    S => output(2),
    C_in => FA_C(1),
    C_out => FA_C(2));

end Behavioral;

```

(FA added previously)

Mux 2 Way 3 Bit

MUX2WAY3BIT.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2Way3Bit is
    Port ( In0 : in STD_LOGIC_VECTOR (2 downto 0);
          In1 : in STD_LOGIC_VECTOR (2 downto 0);
          LoadSelect : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR (2 downto 0));
end Mux2Way3Bit;

```

```

architecture Behavioral of Mux2Way3Bit is
signal s0,s1:std_logic_vector(2 downto 0);
begin
    s0(0) <= (NOT(LoadSelect)) AND In0(0);
    s0(1) <= (NOT(LoadSelect)) AND In0(1);
    s0(2) <= (NOT(LoadSelect)) AND In0(2);

    s1(0) <= (LoadSelect) AND In1(0);
    s1(1) <= (LoadSelect) AND In1(1);
    s1(2) <= (LoadSelect) AND In1(2);

    output <= s0 OR s1;
end Behavioral;

```

Mux 2 Way 4 Bit

MUX2WAY4BIT.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2Way4Bit is
    Port ( In0 : in STD_LOGIC_VECTOR (3 downto 0);
          In1 : in STD_LOGIC_VECTOR (3 downto 0);
          LoadSelect : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR (3 downto 0));
end Mux2Way4Bit;

architecture Behavioral of Mux2Way4Bit is
signal s0,s1:std_logic_vector(3 downto 0);
begin
    s0(0) <= (NOT(LoadSelect)) AND In0(0);
    s0(1) <= (NOT(LoadSelect)) AND In0(1);
    s0(2) <= (NOT(LoadSelect)) AND In0(2);
    s0(3) <= (NOT(LoadSelect)) AND In0(3);

    s1(0) <= (LoadSelect) AND In1(0);
    s1(1) <= (LoadSelect) AND In1(1);
    s1(2) <= (LoadSelect) AND In1(2);
    s1(3) <= (LoadSelect) AND In1(3);

    output <= s0 OR s1;

```

```
end Behavioral;
```

Program Counter

PROGRAMCOUNTER.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ProgramCounter is
    Port ( input : in STD_LOGIC_VECTOR (2 downto 0);
          output : out STD_LOGIC_VECTOR (2 downto 0);
          Clk : in STD_LOGIC;
          Reset : in STD_LOGIC);
end ProgramCounter;

architecture Behavioral of ProgramCounter is

begin

process (Clk) begin
    if (rising_edge(Clk)) then
        if Reset = '1' then
            output <= "000";
        else
            output <= input;
        end if;
    end if;
end process;

end Behavioral;
```

Slow Clock

SLOWCLOCK.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

signal count : integer := 1;
signal clk_status : std_logic := '0';
```



```

begin
  process (Clk_in) begin
    if (rising_edge(Clk_in)) then
      count <= count + 1;
      if (count = 100000000) then -- Roughly 2 to 3 seconds
        clk_status <= not(clk_status);
        Clk_out <= clk_status;
        count <= 1;
      end if;
    end if;
  end process;
end Behavioral;

```

LUT_16_7

LUT_16_7.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity LUT_16_7 is
  Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
        data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is

  type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

  signal sevenSegment_ROM : rom_type := ( "1000000", -- 0
                                           "1111001", -- 1
                                           "0100100", -- 2
                                           "0110000", -- 3
                                           "0011001", -- 4
                                           "0010010", -- 5
                                           "0000010", -- 6
                                           "1111000", -- 7
                                           "0000000", -- 8
                                           "0010000", -- 9
                                           "0001000", -- A
                                           "0000011", -- B
                                           "1000110", -- C
                                           "0100001", -- D
                                           "0000110", -- E
                                           "0001110"); -- F

begin

```

```
data <= sevenSegment_ROM(to_integer(unsigned(address)));

end Behavioral;
```

Simulation Sources

Nano Processor

NANOPROCESSORSIMULATION.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity NanoProcessorSimulation is
-- Port ( );
end NanoProcessorSimulation;

architecture Behavioral of NanoProcessorSimulation is

component NanoProcessor port(
    Clk : in STD_LOGIC;
    Reset : in STD_LOGIC;
    Reg7 : out STD_LOGIC_VECTOR (3 downto 0);
    Zero : out STD_LOGIC;
    Overflow : out STD_LOGIC;
    SevenSegment : out STD_LOGIC_VECTOR(6 downto 0);
    AnodeSelect : out STD_LOGIC_VECTOR(3 downto 0);
    SwitchIn : in STD_LOGIC_VECTOR(3 downto 0));
end component;

SIGNAL Clk,Reset,Zero,Overflow : std_logic;
SIGNAL Reg7,AnodeSelect,SwitchIn : std_logic_vector(3 downto 0);
SIGNAL SevenSegment : std_logic_vector(6 downto 0);

begin

UUT : NanoProcessor port map(
    Clk => Clk,
    Reset => Reset,
    Reg7 => Reg7,
    Zero => Zero,
    Overflow => Overflow,
    SevenSegment => SevenSegment,
    AnodeSelect => AnodeSelect,
    SwitchIn => SwitchIn
);

process
```

```

begin

    Clk <= '0';
    wait for 5ns;

    Clk <= '1';
    wait for 5ns;

end process;

process
begin
    SwitchIn <= "0110";

    Reset <= '1';
    wait for 100ns;


    Reset <= '0';
    wait for 800ns;

    Reset <= '1';
    wait for 50ns;
    Reset <= '0';
    wait;

end process;

end Behavioral;

```

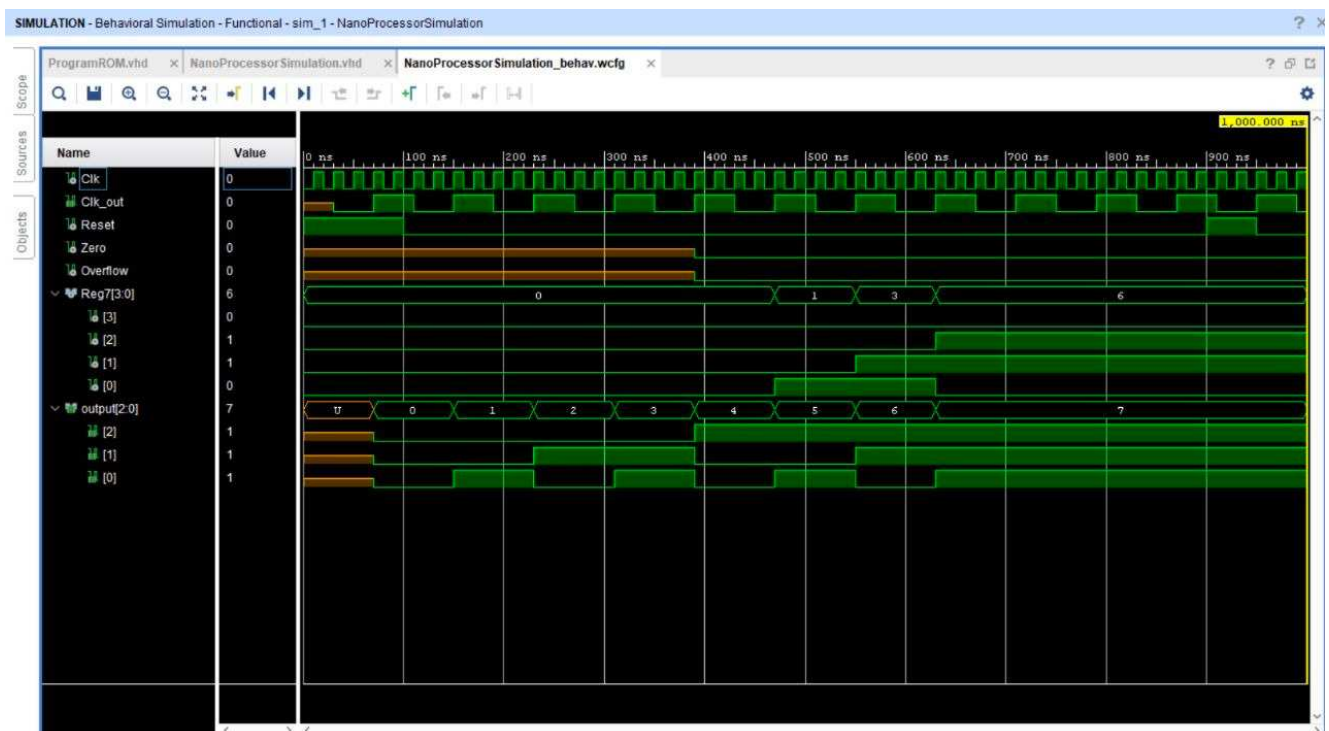

Instruction Decoder

INSTRUCTIONDECODERSIMULATION.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity InstructionDecoderSimulation is
-- Port ( );
end InstructionDecoderSimulation;

architecture Behavioral of InstructionDecoderSimulation is

Component InstructionDecoder
  Port (  InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);
        RegisterCheck : in STD_LOGIC_VECTOR (3 downto 0);
        JumpAddress   : out STD_LOGIC_VECTOR (2 downto 0);
        AddSubSelect  : out STD_LOGIC;
        RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
        LoadSelect    : out STD_LOGIC;
        ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);
        RegASelect    : out STD_LOGIC_VECTOR (2 downto 0);
        RegBSelect    : out STD_LOGIC_VECTOR (2 downto 0);
        JumpFlag      : out STD_LOGIC);
end component;

Signal InstructionBus : STD_LOGIC_VECTOR (11 downto 0);
Signal RegisterCheck, ImmediateValue : STD_LOGIC_VECTOR (3 downto 0);
Signal JumpAddress, RegisterEnable, RegASelect, RegBSelect : STD_LOGIC_VECTOR (2 downto 0);
Signal AddSubSelect, LoadSelect, JumpFlag : STD_LOGIC;

begin

UUT: InstructionDecoder port map(
  InstructionBus => InstructionBus,
  RegisterCheck => RegisterCheck,
  JumpAddress   => JumpAddress,
  AddSubSelect  => AddSubSelect,
  RegisterEnable => RegisterEnable,
  LoadSelect    => LoadSelect,
  ImmediateValue => ImmediateValue,
  RegASelect    => RegASelect,
  RegBSelect    => RegBSelect,
  JumpFlag      => JumpFlag);

process begin
  InstructionBus <= "001011000000";
  wait for 100ns;

  InstructionBus <= "010110000000";
  wait for 100ns;
end process;
end architecture;
```

```


InstructionBus <= "101110001010";
wait for 100ns;

InstructionBus <= "110100000111";
wait;

end process;

end Behavioral;

```

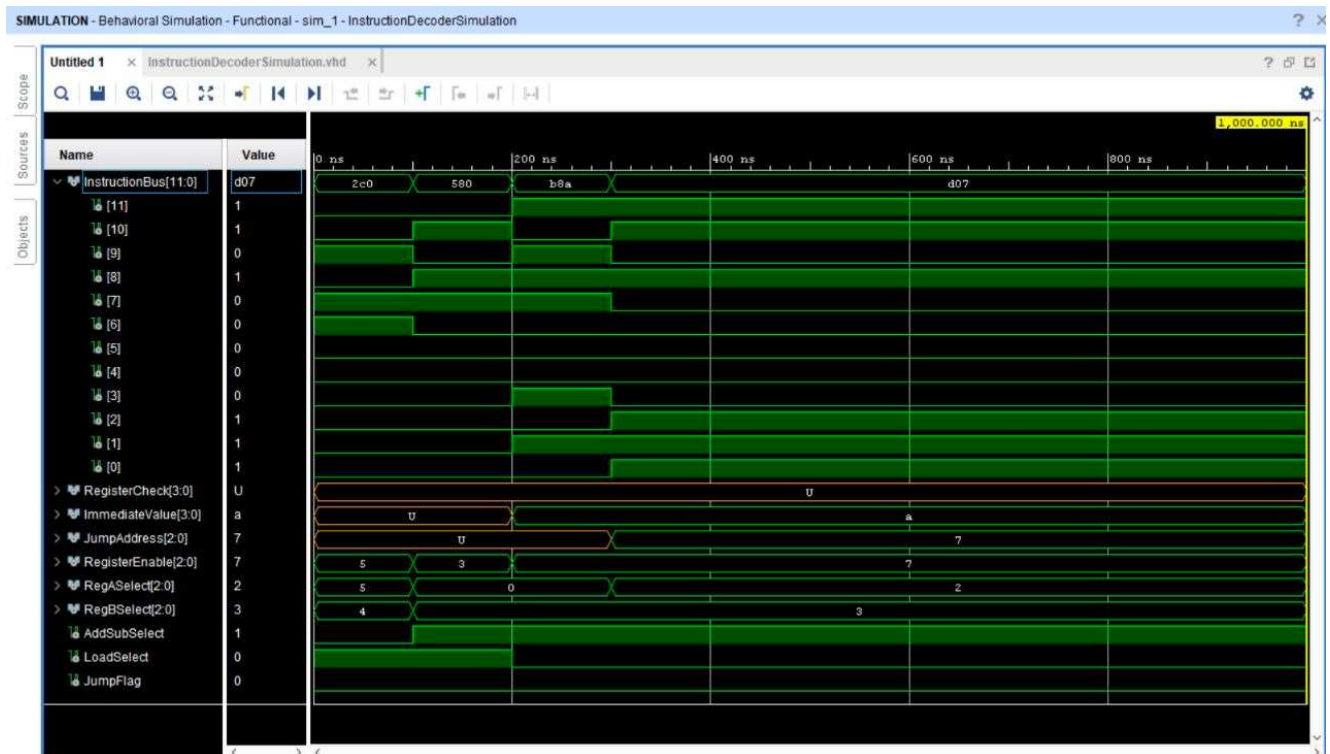

Program ROM

PROGRAMROMSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ProgramROMSimulation is
-- Port ( );
end ProgramROMSimulation;

architecture Behavioral of ProgramROMSimulation is

component ProgramROM
    Port ( MemorySelect : in STD_LOGIC_VECTOR (2 downto 0);
          InstructionBus : out STD_LOGIC_VECTOR (11 downto 0));

```

```

end component;

SIGNAL MemorySelect : STD_LOGIC_VECTOR (2 downto 0);
SIGNAL InstructionBus : STD_LOGIC_VECTOR (11 downto 0);

begin

UUT : ProgramROM port map(
    MemorySelect => MemorySelect,
    InstructionBus => InstructionBus
);

process
begin

MemorySelect <= "000";
wait for 100ns;

MemorySelect <= "001";
wait for 100ns;

MemorySelect <= "010";
wait for 100ns;

MemorySelect <= "011";
wait for 100ns;

MemorySelect <= "100";
wait for 100ns;

MemorySelect <= "101";
wait for 100ns;


MemorySelect <= "110";
wait for 100ns;

MemorySelect <= "111";
wait;

end process;

end Behavioral;

```

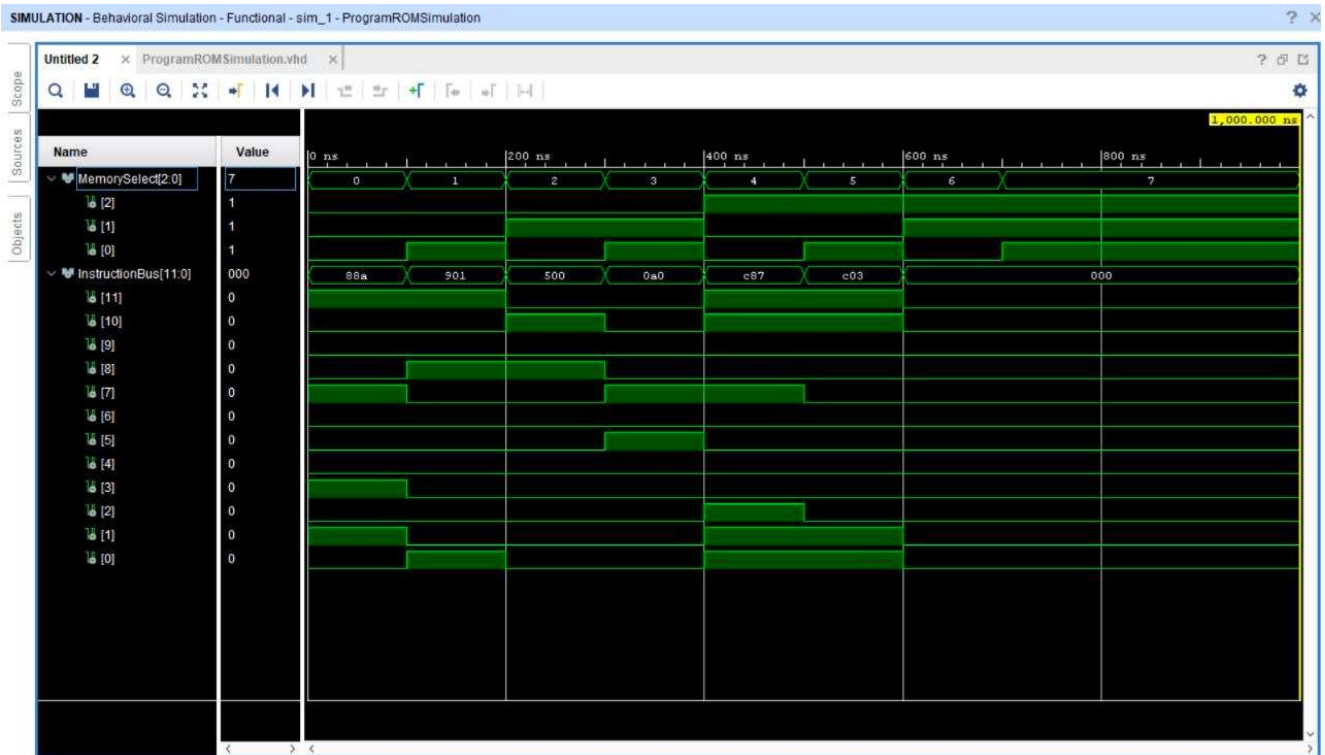

Register Bank

REGISTERBANKSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RegisterBankSimulation is
-- Port ( );
end RegisterBankSimulation;

architecture Behavioral of RegisterBankSimulation is

component RegisterBank port(
    RegisterIn : in STD_LOGIC_VECTOR (3 downto 0);
    Clk : in STD_LOGIC;
    output0 : out STD_LOGIC_VECTOR (3 downto 0);
    output1 : out STD_LOGIC_VECTOR (3 downto 0);
    output2 : out STD_LOGIC_VECTOR (3 downto 0);
    output3 : out STD_LOGIC_VECTOR (3 downto 0);
    output4 : out STD_LOGIC_VECTOR (3 downto 0);
    output5 : out STD_LOGIC_VECTOR (3 downto 0);
    output6 : out STD_LOGIC_VECTOR (3 downto 0);
    output7 : out STD_LOGIC_VECTOR (3 downto 0);
    RegisterEn : in STD_LOGIC_VECTOR (2 downto 0);
    Reset : in STD_LOGIC);
end component;

```

```

SIGNAL RegisterIn, output0, output1, output2, output3, output4, output5, output6, output7
: std_logic_vector(3 downto 0);
SIGNAL RegisterEn : std_logic_vector(2 downto 0);
SIGNAL Clk,Reset : std_logic;

begin

UUT: RegisterBank port map(
    RegisterIn => RegisterIn,
    Clk => Clk,
    output0 => output0,
    output1 => output1,
    output2 => output2,
    output3 => output3,
    output4 => output4,
    output5 => output5,
    output6 => output6,
    output7 => output7,
    RegisterEn => RegisterEn,
    Reset => Reset
);

process begin

    Clk <= '0';
    wait for 5ns;

    Clk <= '1';
    wait for 5ns;

end process;

process begin

    Reset <= '0';

    RegisterEn <= "001";
    RegisterIn <= "1010";
    wait for 100 ns;

    RegisterEn <= "010";
    RegisterIn <= "0110";
    wait for 100 ns;

    RegisterEn <= "011";
    RegisterIn <= "1111";
    wait for 100 ns;

    RegisterEn <= "100";
    RegisterIn <= "0011";
    wait for 100 ns;

```



```

RegisterEn <= "101";
RegisterIn <= "1100";
wait for 100 ns;

RegisterEn <= "110";
RegisterIn <= "0100";
wait for 100 ns;

RegisterEn <= "111";
RegisterIn <= "0111";
wait for 100 ns;


RegisterEn <= "010";
RegisterIn <= "0000";
wait for 100 ns;

Reset <= '1';
wait;

end process;

end Behavioral;

```

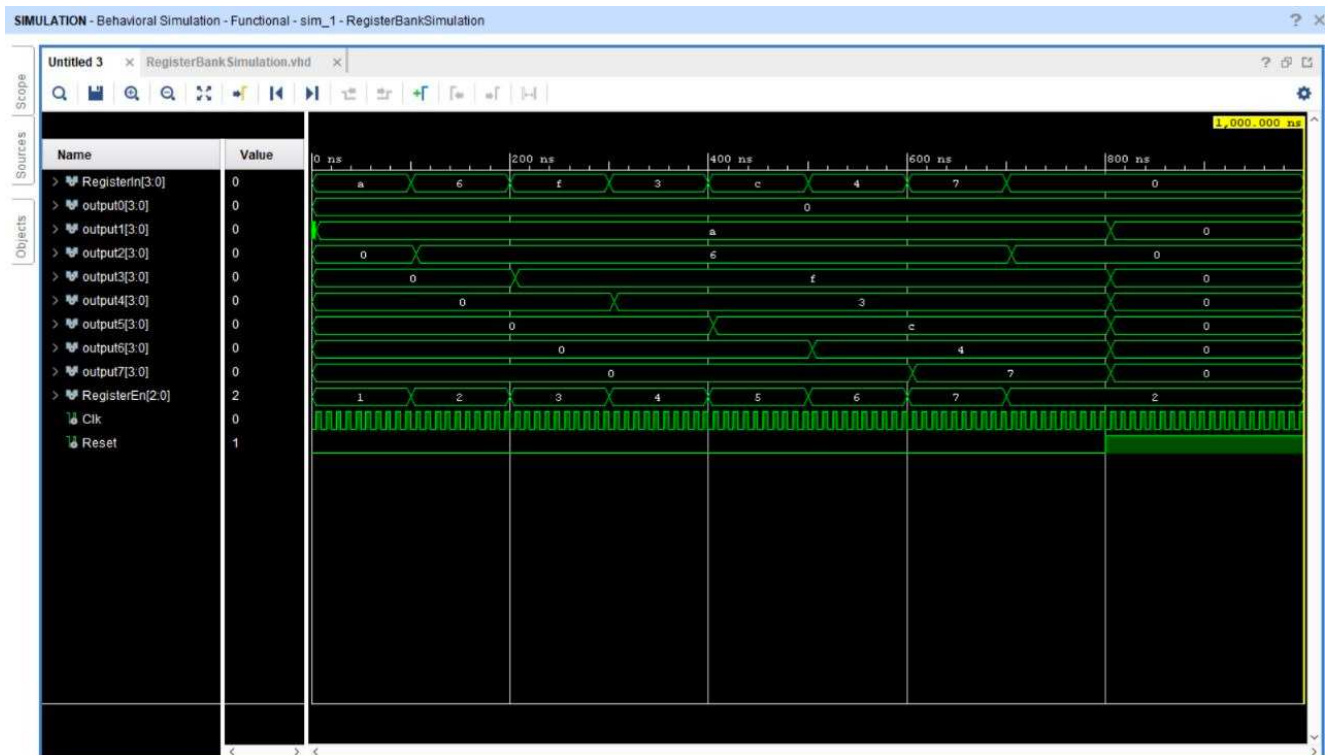

Add Sub Unit

ADDSUBSIMULATION.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity AddSubSimulation is
-- Port ( );
end AddSubSimulation;

architecture Behavioral of AddSubSimulation is

component AddSubUnit
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          S : out STD_LOGIC_VECTOR (3 downto 0);
          AddSubSelect : in STD_LOGIC;
          Overflow : out STD_LOGIC;
          Zero : out STD_LOGIC);
end component;

SIGNAL A,B,S : std_logic_vector(3 downto 0);
SIGNAL AddSubSelect,Overflow,Zero : std_logic;

begin

UUT : AddSubUnit
    port map(
        A => A,
        B => B,
        S => S,
        AddSubSelect => AddSubSelect,
        Overflow => Overflow,
        Zero => Zero
    );

process
begin

A <= ("0001");
B <= ("0001");
AddSubSelect <= '0';
wait for 100ns;

A <= ("0010");
B <= ("0001");
AddSubSelect <= '1';
wait for 100ns;

A <= ("1001");
B <= ("0111");
```

```


AddSubSelect <= '0';
wait for 100ns;

A <= ("0001");
B <= ("0001");
AddSubSelect <= '1';
wait;

end process;

end Behavioral;

```

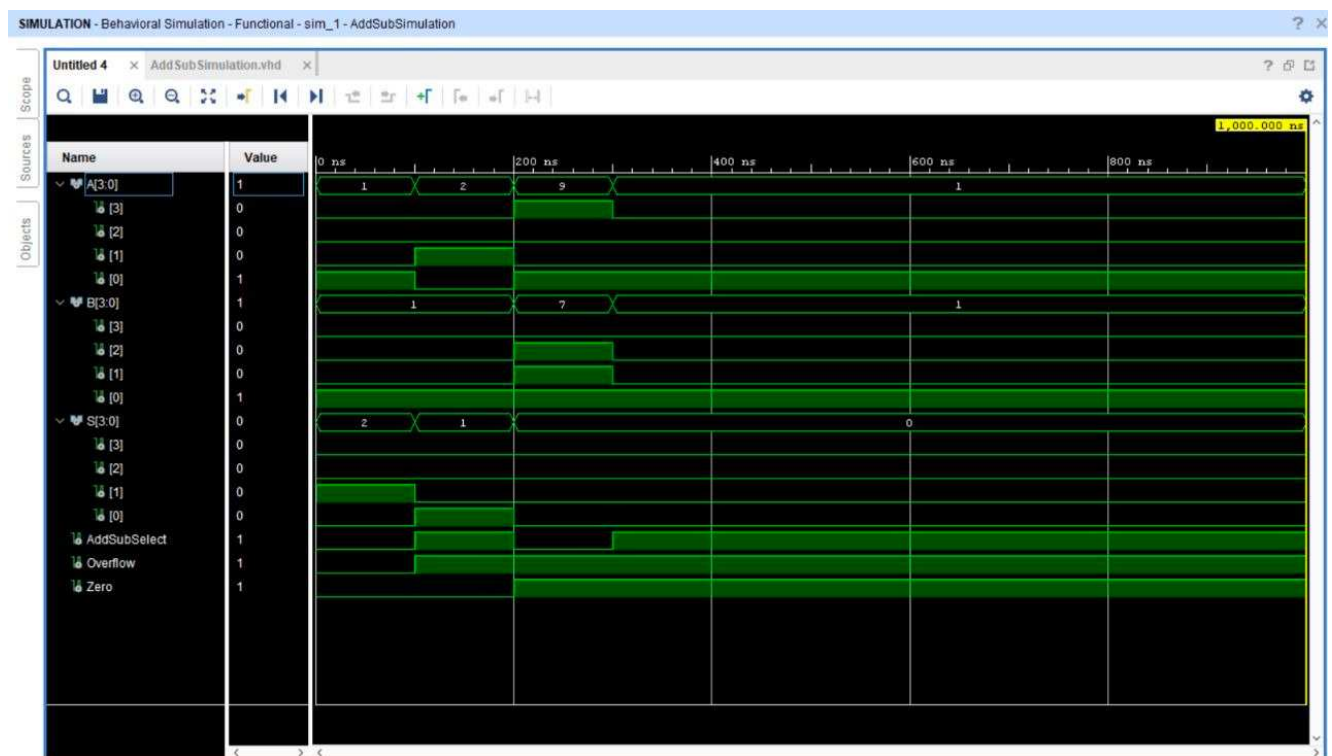

Mux 8 Way 4 Bit

MUX8WAY4BITSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux8Way4BitSimulation is
-- Port ( );
end Mux8Way4BitSimulation;

architecture Behavioral of Mux8Way4BitSimulation is

component Mux8Way4Bit Port(
    In0 : in STD_LOGIC_VECTOR (3 downto 0);
    In1 : in STD_LOGIC_VECTOR (3 downto 0);

```

```

        In2 : in STD_LOGIC_VECTOR (3 downto 0);
        In3 : in STD_LOGIC_VECTOR (3 downto 0);
        In4 : in STD_LOGIC_VECTOR (3 downto 0);
        In5 : in STD_LOGIC_VECTOR (3 downto 0);
        In6 : in STD_LOGIC_VECTOR (3 downto 0);
        In7 : in STD_LOGIC_VECTOR (3 downto 0);
        OutMux : out STD_LOGIC_VECTOR (3 downto 0);
        Control : in STD_LOGIC_VECTOR (2 downto 0));
end component;

SIGNAL In0,In1,In2,In3,In4,In5,In6,In7,OutMux : std_logic_vector(3 downto 0);
SIGNAL Control : std_logic_vector(2 downto 0);

begin

UUT : Mux8Way4Bit Port map(
    In0 => In0,
    In1 => In1,
    In2 => In2,
    In3 => In3,
    In4 => In4,
    In5 => In5,
    In6 => In6,
    In7 => In7,
    OutMux => OutMux,
    Control => Control
);

process
begin

In0 <= "1111";
In1 <= "1110";
In2 <= "1101";
In3 <= "1100";
In4 <= "1011";
In5 <= "1010";
In6 <= "1001";
In7 <= "1000";

Control <= "000";
wait for 100ns;

Control <= "001";
wait for 100ns;

Control <= "010";
wait for 100ns;

Control <= "011";
wait for 100ns;

```

```

Control <= "100";
wait for 100ns;

Control <= "101";
wait for 100ns;


Control <= "110";
wait for 100ns;

Control <= "111";
wait;

end process;

end Behavioral;

```

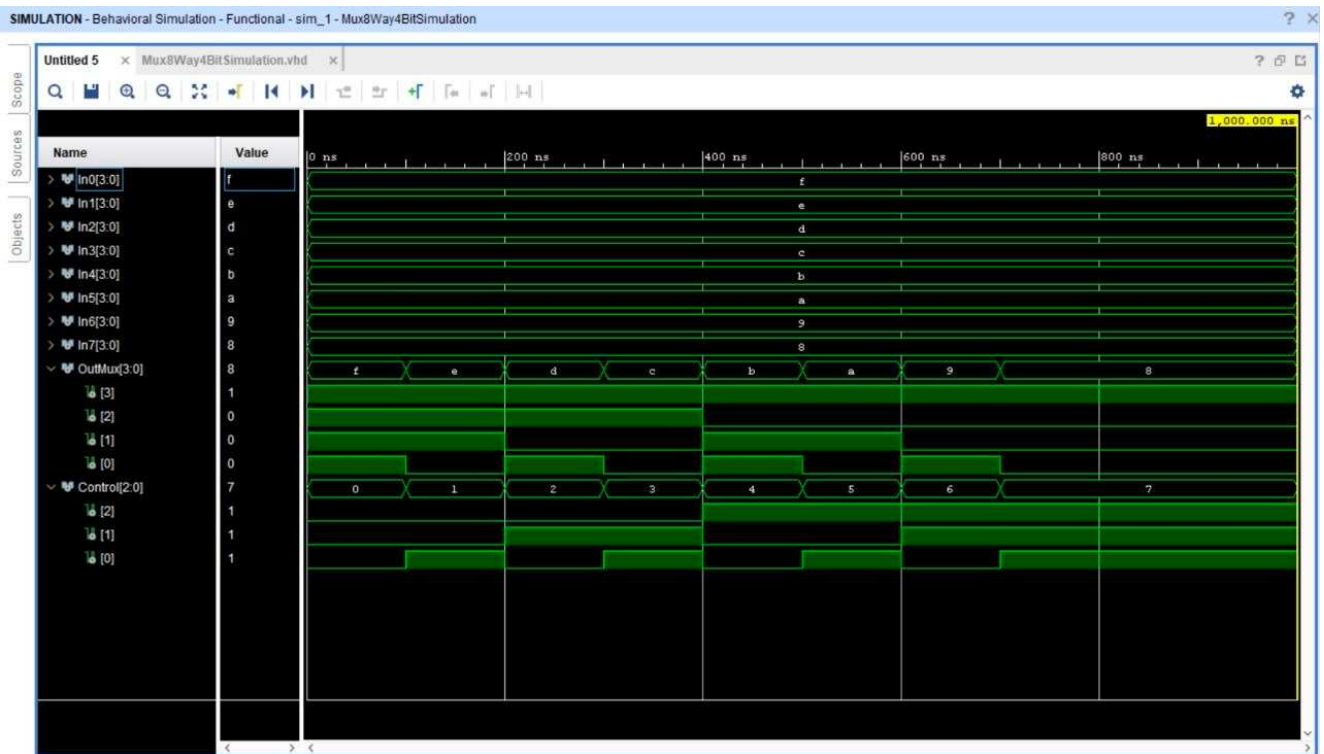

Adder 3 bit

ADDER3BITSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Adder3BitSimulation is
-- Port ( );
end Adder3BitSimulation;

architecture Behavioral of Adder3BitSimulation is
component Adder3Bit Port (

```

```

        A : in STD_LOGIC_VECTOR (2 downto 0);
        B : in STD_LOGIC_VECTOR (2 downto 0);
        output : out STD_LOGIC_VECTOR (2 downto 0));

end component;

SIGNAL A,B,output : std_logic_vector( 2 downto 0);

begin

UUT : Adder3Bit port map(
    A => A,
    B => B,
    output => output
);

process
begin

A <= "000";
B <= "001";

wait for 100ns;

A <= "001";
B <= "001";

wait for 100ns;

A <= "010";
B <= "001";

wait for 100ns;

A <= "011";
B <= "001";

wait for 100ns;

A <= "100";
B <= "001";

wait for 100ns;

A <= "101";
B <= "001";

wait for 100ns;

```

```

A <= "110";
B <= "001";

wait for 100ns;


A <= "111";
B <= "001";

wait;

end process;

end Behavioral;

```

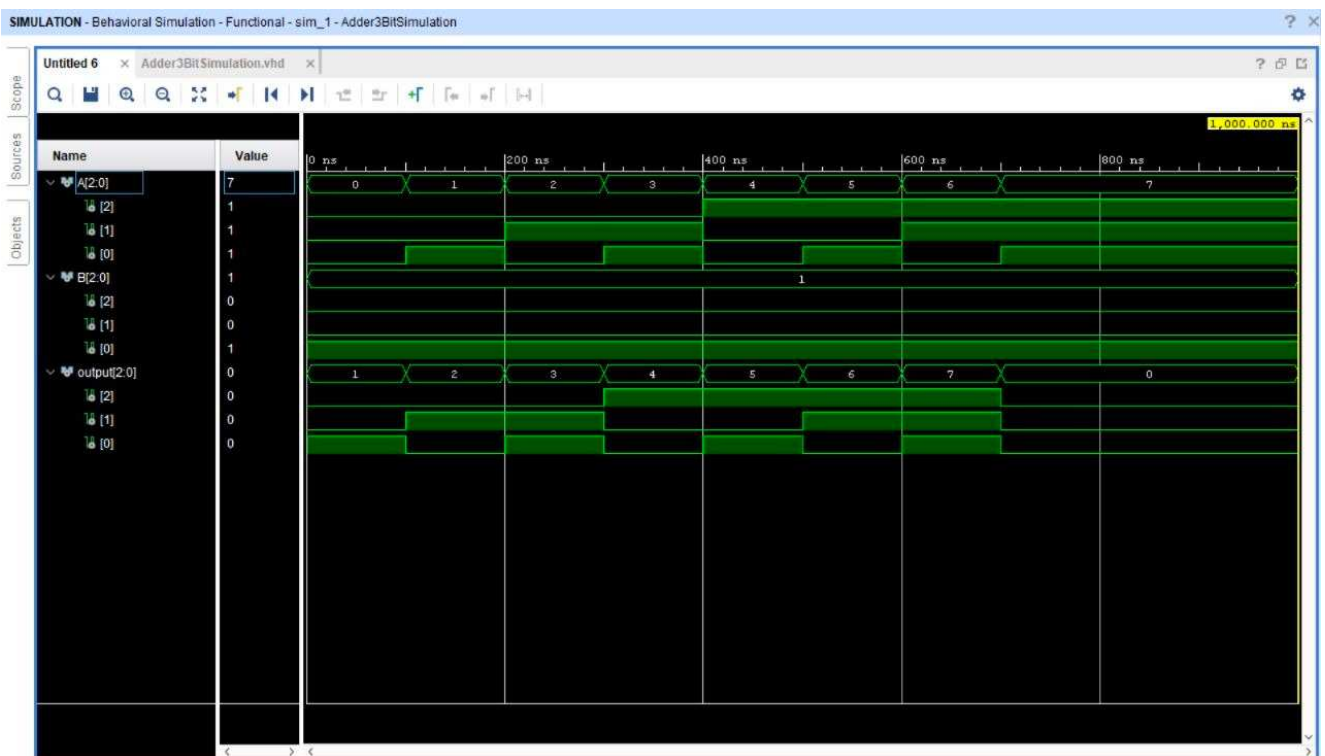

Mux 2 Way 3 Bit

MUX2WAY3BITSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2Way3BitSimulation is
-- Port ( );
end Mux2Way3BitSimulation;

architecture Behavioral of Mux2Way3BitSimulation is

component Mux2Way3Bit Port(
    In0 : in STD_LOGIC_VECTOR (2 downto 0);

```

```

        In1 : in STD_LOGIC_VECTOR (2 downto 0);
        LoadSelect : in STD_LOGIC;
        output : out STD_LOGIC_VECTOR (2 downto 0));
end component;

SIGNAL In0,In1,output : std_logic_vector(2 downto 0);
SIGNAL LoadSelect : std_logic;

begin

UUT : Mux2Way3Bit Port map(
    In0 => In0,
    In1 => In1,
    LoadSelect => LoadSelect,
    output => output
);

process
begin


In0 <= "101";
In1 <= "010";

LoadSelect <= '0';
wait for 500ns;
LoadSelect <= '1';
wait;

end process;

end Behavioral;

```

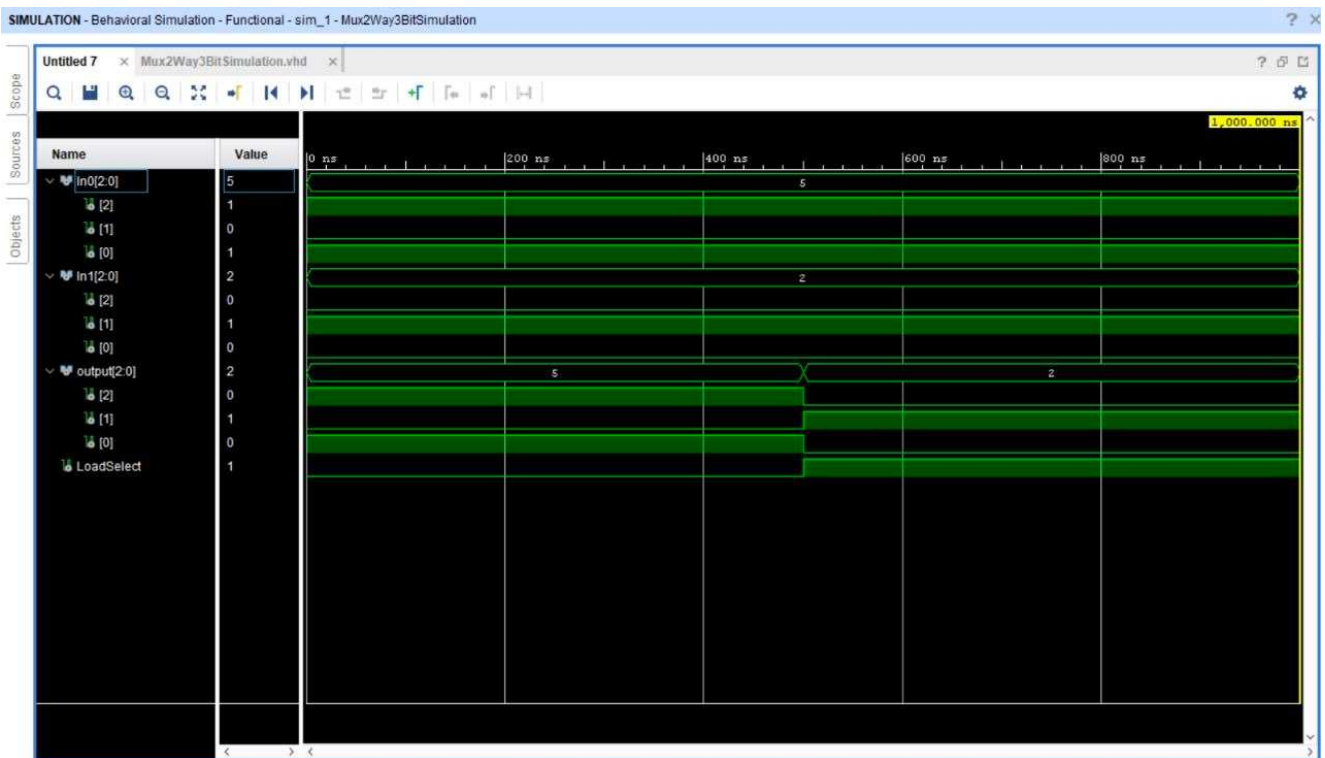Mux 2 Way 4 Bit

MUX2WAY4BITSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2Way4BitSimulation is
    -- Port ( );
end Mux2Way4BitSimulation;

architecture Behavioral of Mux2Way4BitSimulation is

    component Mux2Way4Bit Port(
        In0 : in STD_LOGIC_VECTOR (3 downto 0);
        In1 : in STD_LOGIC_VECTOR (3 downto 0);
        LoadSelect : in STD_LOGIC;
        output : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    SIGNAL In0,In1,output : std_logic_vector(3 downto 0);
    SIGNAL LoadSelect : std_logic;

begin

    UUT : Mux2Way4Bit Port map(
        In0 => In0,
        In1 => In1,

```

```

LoadSelect => LoadSelect,
output => output
);

process
begin


In0 <= "1001";
In1 <= "0110";

LoadSelect <= '0';
wait for 500ns;
LoadSelect <= '1';
wait;

end process;

end Behavioral;

```

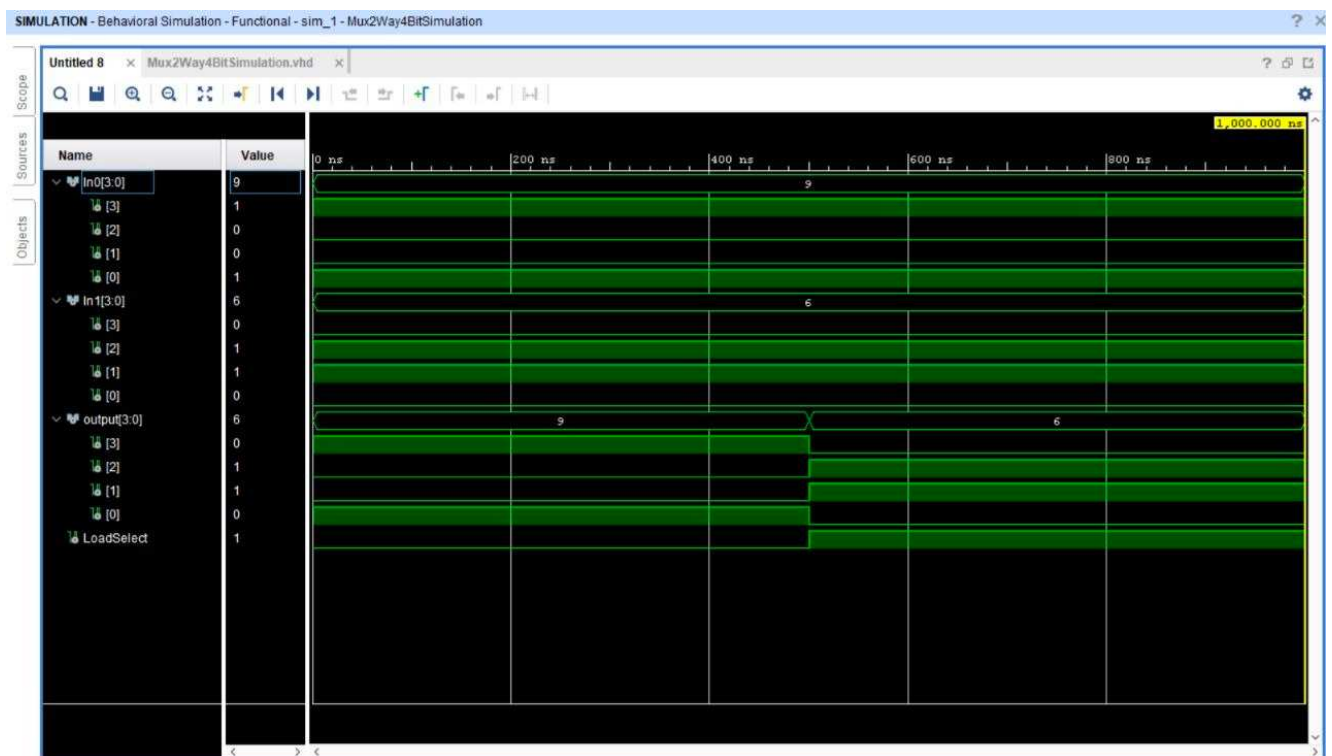

Program Counter

PROGRAMCOUNTERSIMULATION.VHD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ProgramCounterSimulation is
-- Port ( );

```

```

end ProgramCounterSimulation;

architecture Behavioral of ProgramCounterSimulation is

component ProgramCounter
    Port ( input : in STD_LOGIC_VECTOR (2 downto 0);
          output : out STD_LOGIC_VECTOR (2 downto 0);
          Clk : in STD_LOGIC;
          Reset : in STD_LOGIC);
end component;

SIGNAL input,output : std_logic_vector (2 downto 0);
SIGNAL Clk,Reset : std_logic;

begin

UUT : ProgramCounter port map(
    input => input,
    output => output,
    Clk => Clk,
    Reset => Reset
);

process
begin
Clk <= '0';
wait for 50ns;

Clk <= '1';
wait for 50ns;

end process;

process
begin

reset <= '0';


input <= "101";
wait for 200ns;

input <= "010";
wait for 200ns;

reset <= '1';
wait;

```
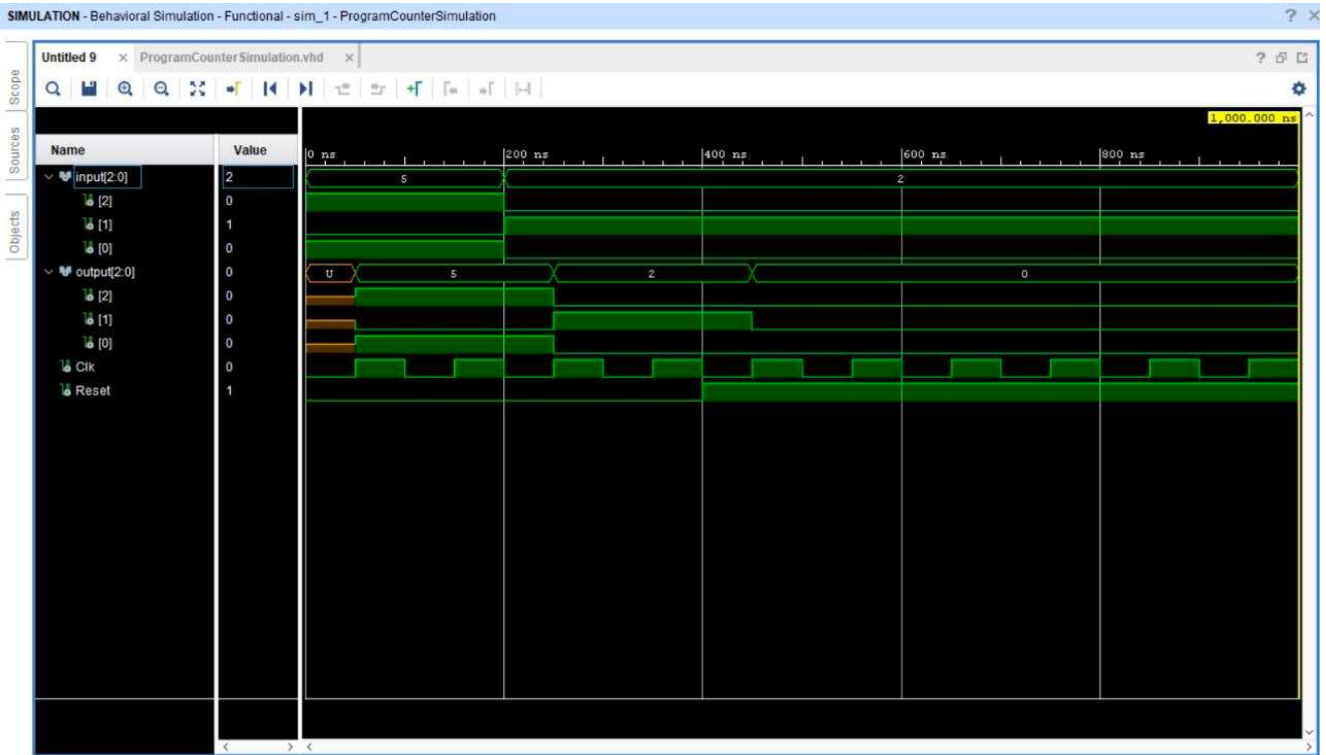
```
end process;  
  
end Behavioral;
```



CONCLUSIONS

From this lab we were able to sharpen our knowledge on the VHDL, Vivado and Computer digital design. Also, we were able to design and develop a 4-bit arithmetic unit that can add and subtract signed integers, decode instructions to activate necessary components on the processor, design and develop k-way b-bit multiplexers. verify their functionality via simulation and on the development board. This gave a good understanding on Nano Processors.

CONTRIBUTION FROM TEAM MEMBERS

Gathsara J.A.S –

- Making Design Sources and coding them.
- Made Upgrades on Reprogrammable design.

Gallage D. –

- Making the simulation files and testing the test bench.
- Made Upgrades on Additional Instructions adding.
- Made Seven Segment Up and Running.

NUMBER OF HOURS SPENT

Working about 28 hours Total.